



بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

In the name of Allah, the Most Merciful, the Most Kind

Date: 08-11-2021

BCS 103

Digital Logic & Computer Architecture

Lecture 27 and 28

IN THE LAST LECTURE

We have discussed

Adders

- **Half Adder**
- **Full Adder**

n-bit Ripple Carry Adder

IN THE TODAY'S LECTURE

Today we will discuss about:

Subtractor

- **Half Subtractor**
- **Full Subtractor**

Parallel Binary Subtractor

Half Subtractor

Half Subtractor

TYPES OF BINARY SUBTRACTOR

- Half Subtractor
- Full Subtractor

Half Subtractor:

- It is a combinational circuit with two inputs and two outputs.
- Two inputs are A (minuend), B (subtrahend) and two outputs are D (difference) and B_o (borrow out).
- It is used to perform subtraction of two bits.

Half Subtractor

RULES FOR BINARY SUBTRACTION

$$0 - 0 = 0$$

$$0 - 1 = 1 \text{ (with borrow 1)}$$

$$1 - 0 = 1$$

$$1 - 1 = 0$$

NOTE: In the second case (0-1)
it is necessary to borrow a 1.

Half Subtractor

TRUTH TABLE OF HALF-SUBTRACTOR


INPUTS		OUTPUTS	
Minuend (A)	Subtrahend (B)	Difference (D)	Borrow (B_o)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Half Subtractor


TRUTH TABLE OF HALF-SUBTRACTOR

INPUTS		OUTPUTS	
Minuend (A)	Subtrahend (B)	Difference (D)	Borrow (B_o)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

K-Map for difference (D)

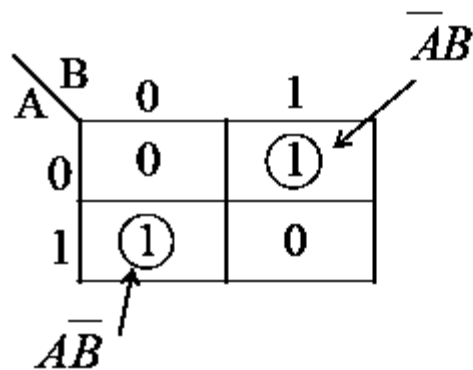

K-Map for Borrow Output (B_o)

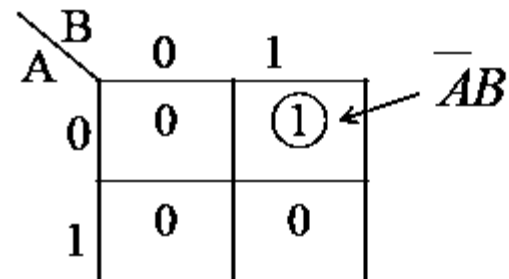


Half Subtractor

From K-maps

$$D = \overline{A}B + A\overline{B}$$

$$B = \overline{A}B$$

HALF SUBTRACTOR USING BASIC GATES:

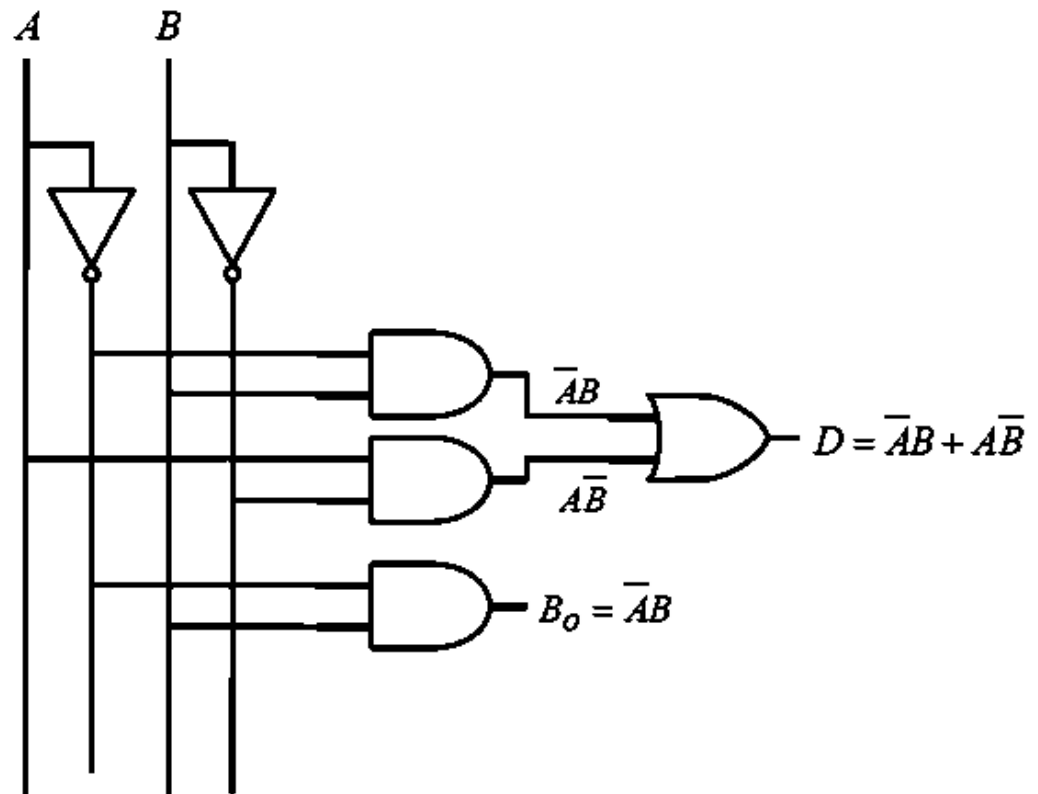


Half Subtractor

From K-maps

$$D = \overline{A}B + A\overline{B}$$


$$B_o = \overline{A}B$$

LOGIC DIAGRAM

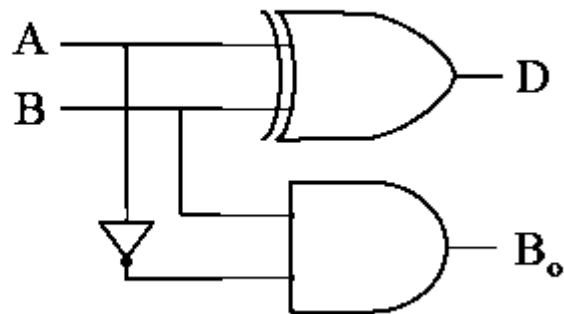


Half Subtractor

LOGIC DIAGRAM:

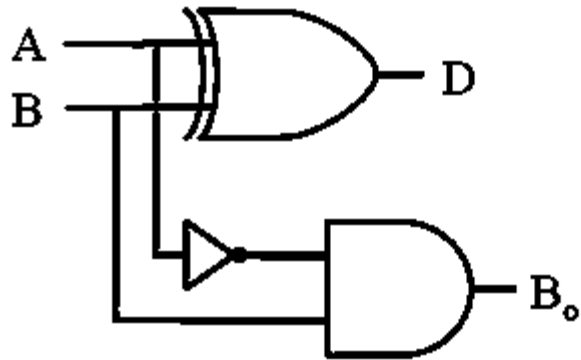

BLOCK DIAGRAM:

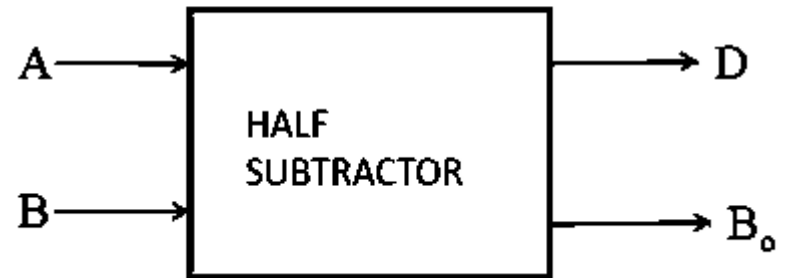

Disadvantage of Half Subtractor:

Half subtractor can only perform the subtraction of two binary bits. But while performing the subtraction, it does not take into account the borrow of the lower significant stage.

Full Subtractor

Full Subtractor

- Full subtractor is a combinational circuit.
- It performs subtraction involving three bits (inputs)
 1. Minuend bit (X)
 2. Subtrahend bit (Y)
 3. Borrow from the previous stage (B_{in})
- It has two outputs
 1. Difference (D)
 2. Borrow out B_{out} .

Full Subtractor

TRUTH TABLE:

INPUTS			OUTPUTS	
X	Y	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Full Subtractor

TRUTH TABLE:

INPUTS			OUTPUTS	
X	Y	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

K-Map For Difference Output (D)

		YB _{in}			
		00	01	11	10
X	0	0	①	0	①
	1	①	0	①	0

$$D = \overline{X}\overline{Y}B_{in} + \overline{X}Y\overline{B_{in}} + X\overline{Y}\overline{B_{in}} + XYB_{in}$$

Full Subtractor

TRUTH TABLE:

INPUTS			OUTPUTS	
X	Y	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

K-Maps For Borrow Output (B_{out})

X \ YB _{in}					
		00	01	11	10
0	0	0	1	1	1
1	0	0	0	1	0

$$B_{out} = \overline{X}Y + \overline{X}B_{in} + YB_{in}$$

Full Subtractor

$$D = \overline{X}\overline{Y}B_{in} + \overline{X}Y\overline{B_{in}} + X\overline{Y}\overline{B_{in}} + XYB_{in}$$


$$D = (\overline{X}\overline{Y} + XY)B_{in} + (\overline{X}Y + X\overline{Y})\overline{B_{in}}$$

$$D = (\overline{X \oplus Y})B_{in} + (X \oplus Y)\overline{B_{in}}$$

$$D = X \oplus Y \oplus B_{in}$$


Full Subtractor

RELIZATION OF FULL SUBTRACTOR:

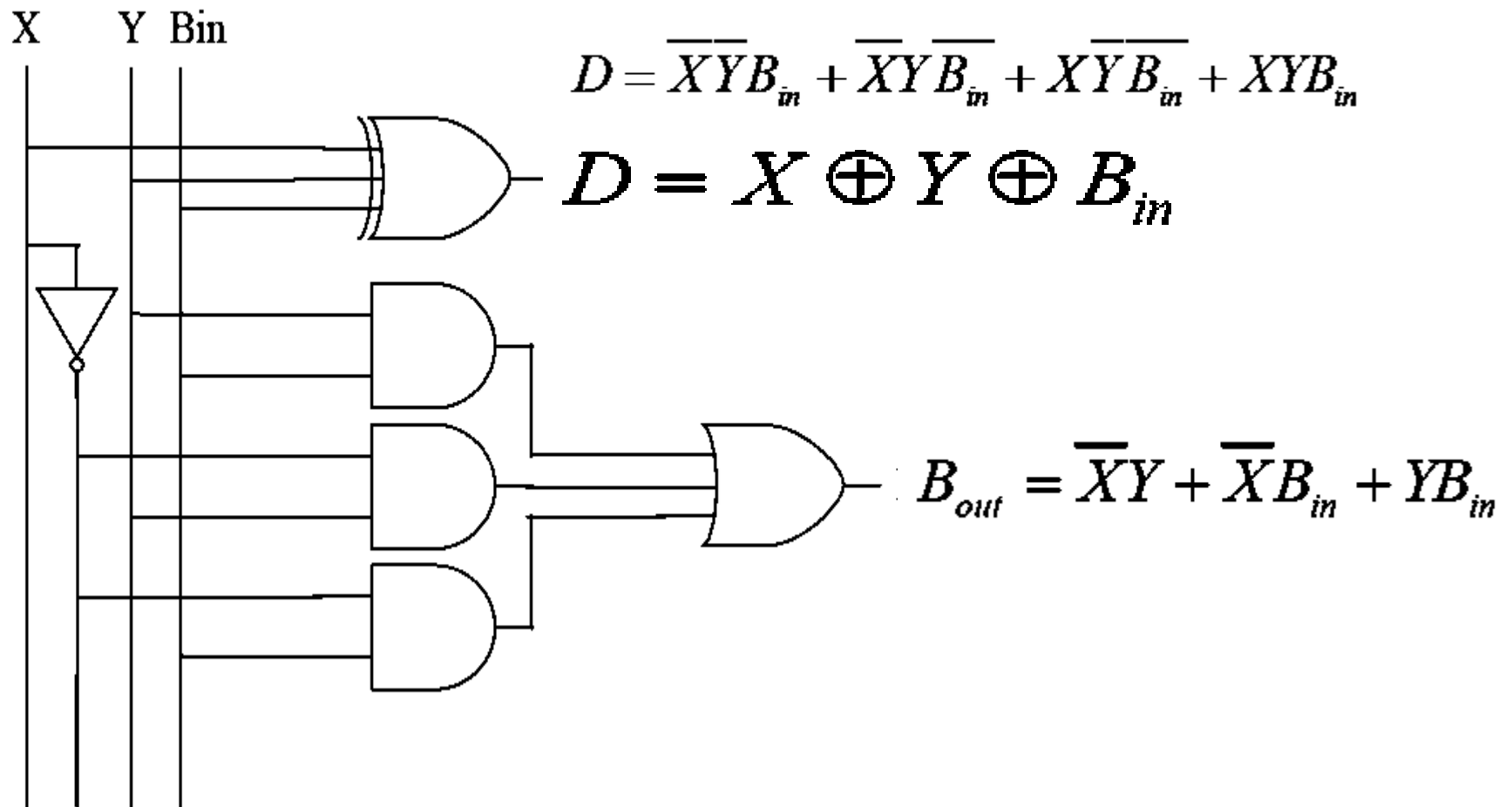

Full Subtractor

$$D = A \oplus B \oplus C$$

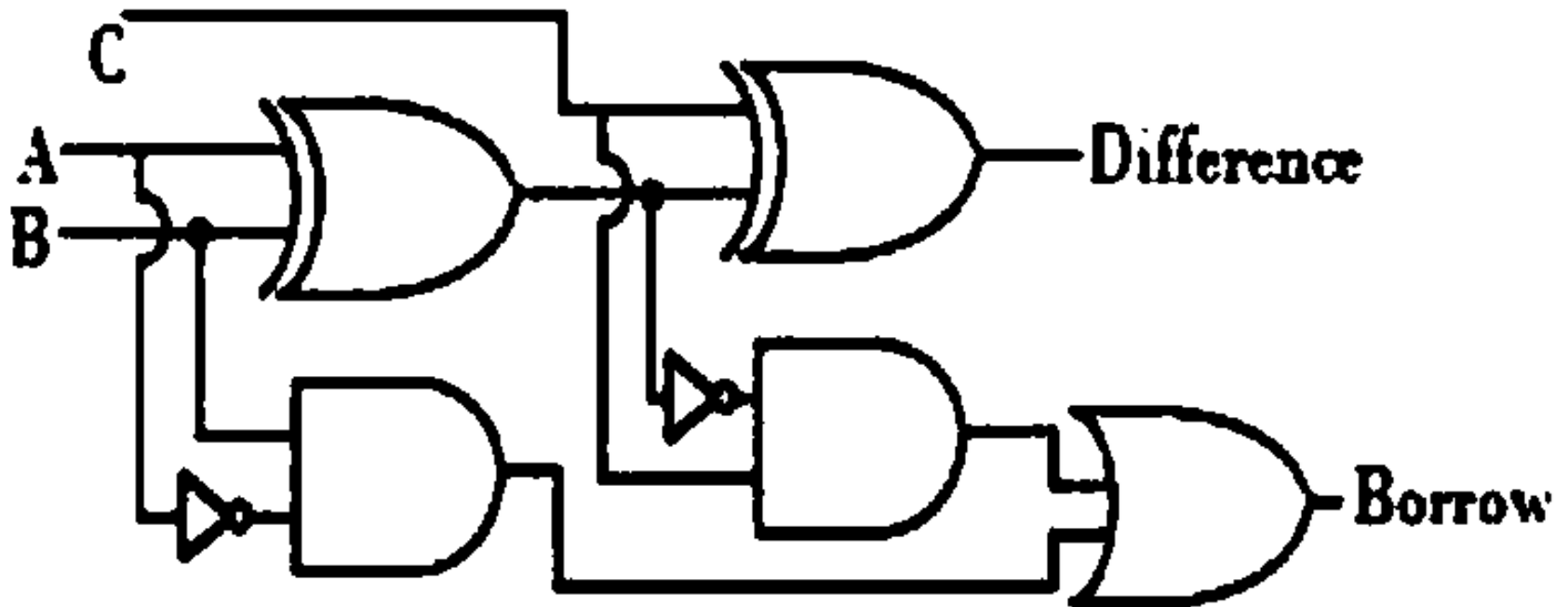


$$B_{(out)} = BC + (B \oplus C) A$$

Parallel Binary Subtractor

Parallel binary subtractor can be implemented by cascading several full-subtractors.

Next slide shows the block level representation of a 4-bit parallel binary subtractor, which subtracts 4-bit $b_3b_2b_1b_0$ from 4-bit $a_3a_2a_1a_0$. It has 4-bit difference output $D_3D_2D_1D_0$ with borrow output $B(out)$.

Parallel Binary Subtractor

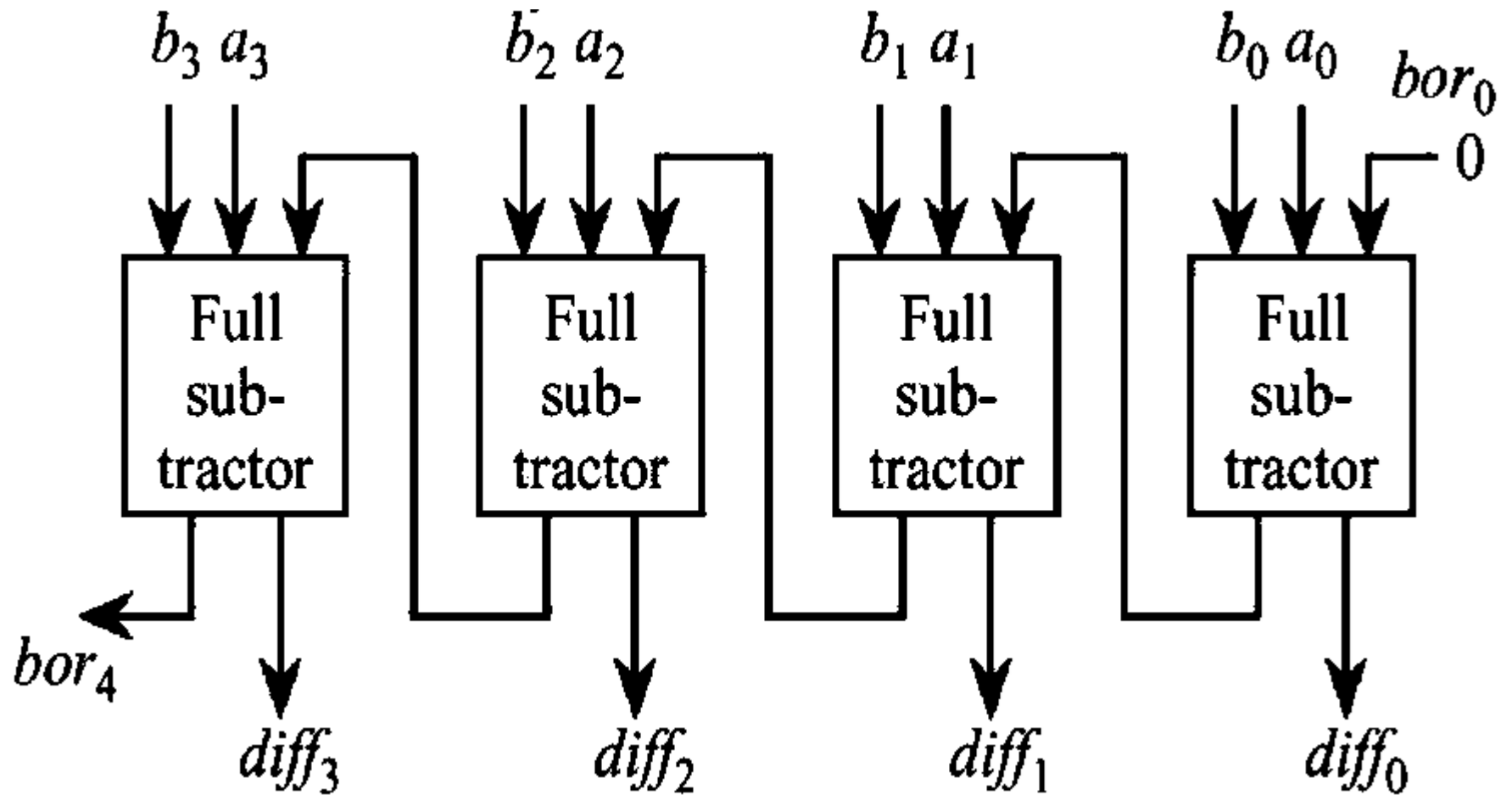

Thanks