



بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

*In the name of Allah, the Most Merciful, the Most Kind*

Date: 12-11-2021

# **BCS 103**

## **Digital Logic & Computer Architecture**

**Lecture 31 and 32**

# LAST LECTURE

In the Last Lecture

- **Decoder (2x4)**
- **Decoder (3x8)**
- **Encoder (4x2)**
- **Decimal to BCD Encoder**

# TODAY'S LECTURE

Today we will discuss about:


- **Multiplexer**
- **De-multiplexer**

# Multiplexer


# What is a Multiplexer (MUX)?

- A MUX is a digital switch that has multiple inputs (sources) and a single output (destination).
- The select lines determine which input is connected to the output.
- MUX Types
  - 2-to-1 (1 select line)
  - 4-to-1 (2 select lines)
  - 8-to-1 (3 select lines)
  - 16-to-1 (4 select lines)



Multiplexer  
Block Diagram

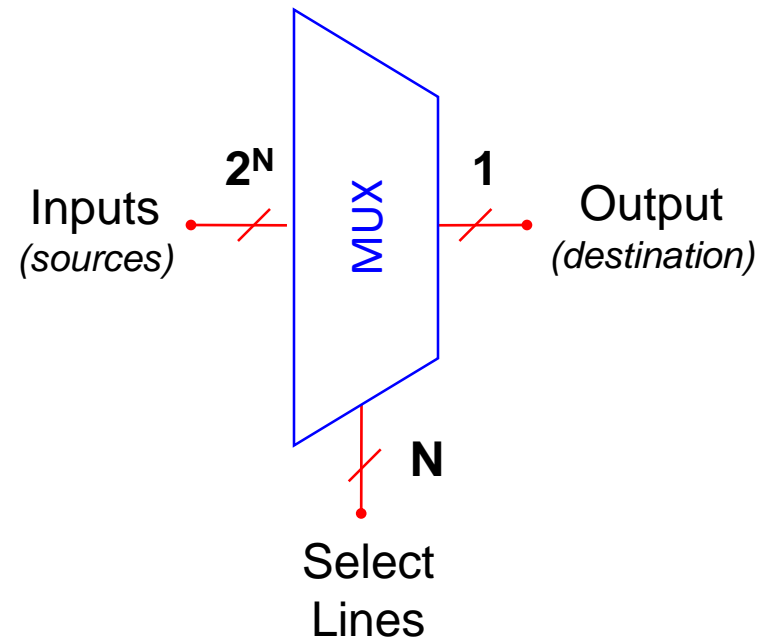

# Typical Application of a MUX

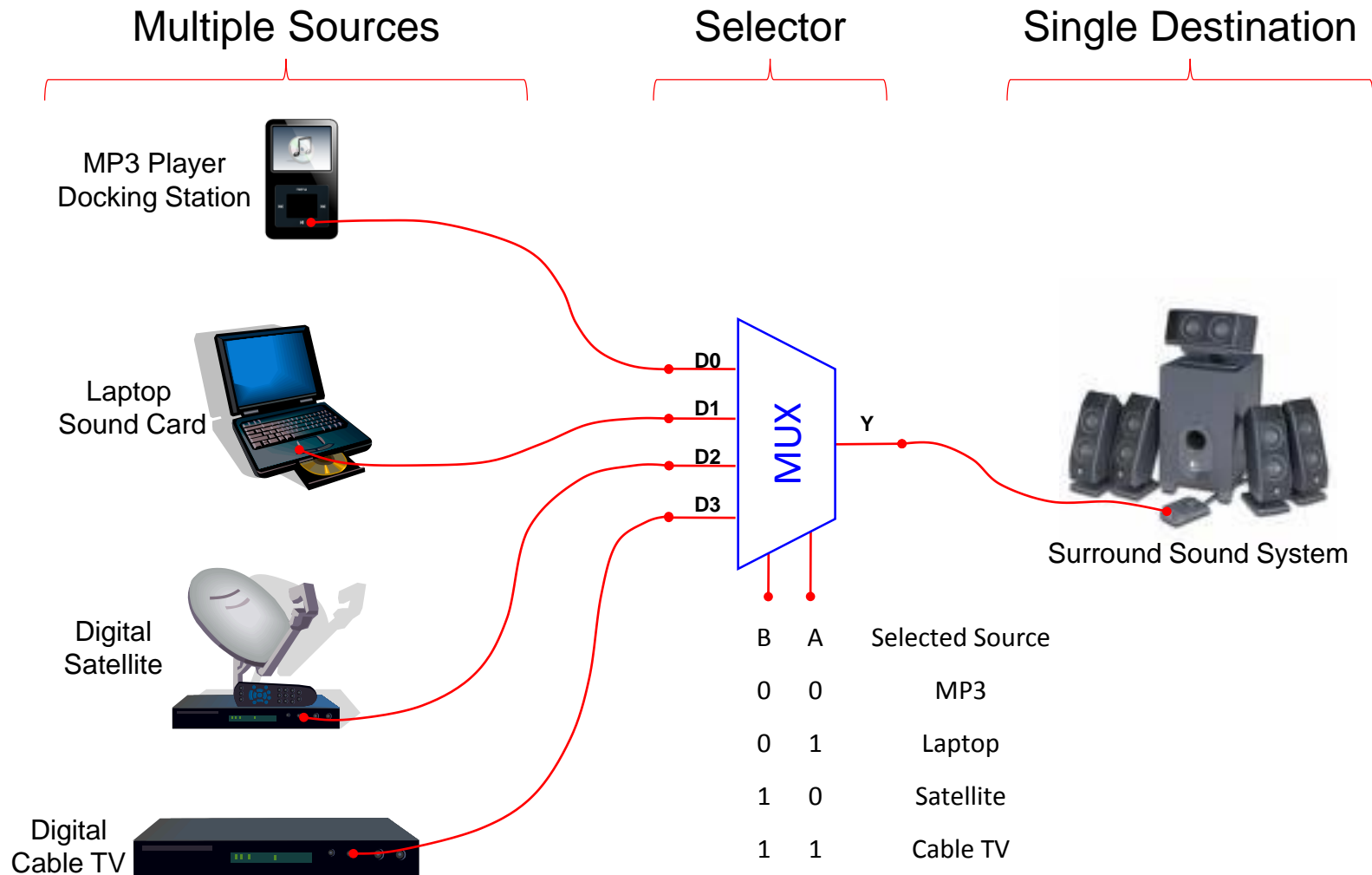

# 4-to-1 Multiplexer (MUX)

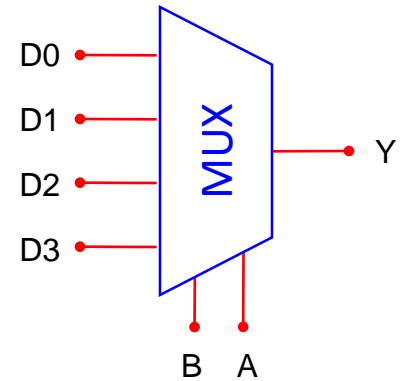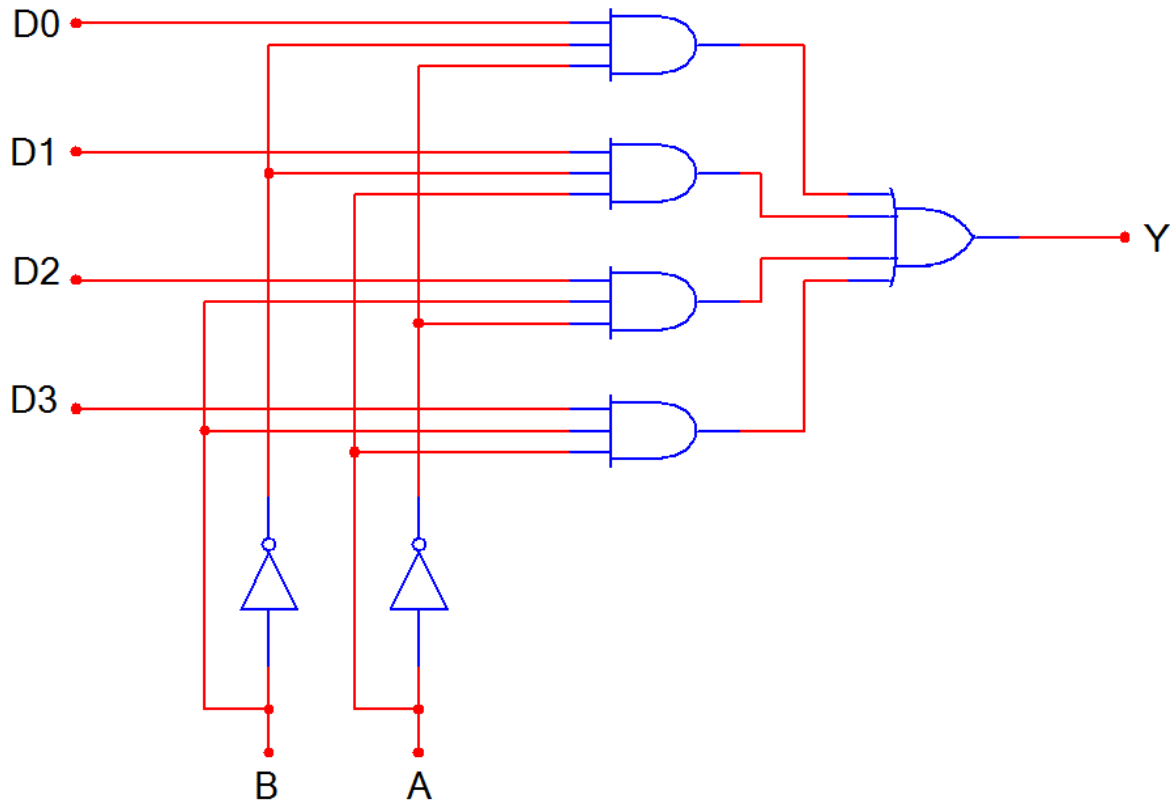

B	A	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3


# De-Multiplexer




# What is a De-Multiplexer (DEMUX)?

- A DEMUX is a digital switch with a single input (source) and a multiple outputs (destinations).
- The select lines determine which output the input is connected to.
- DEMUX Types
  - 1-to-2 (1 select line)
  - 1-to-4 (2 select lines)
  - 1-to-8 (3 select lines)
  - 1-to-16 (4 select lines)



De-Multiplexer  
Block Diagram

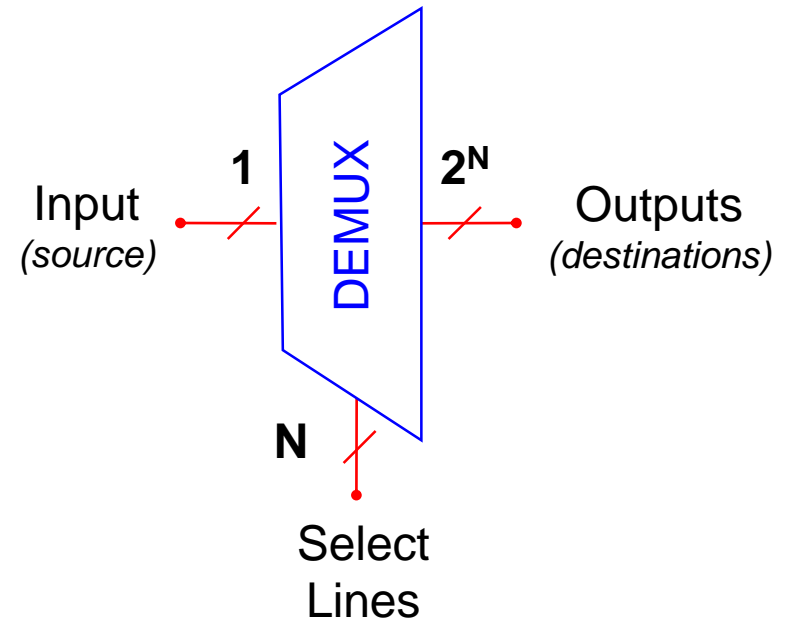

# Typical Application of a DEMUX

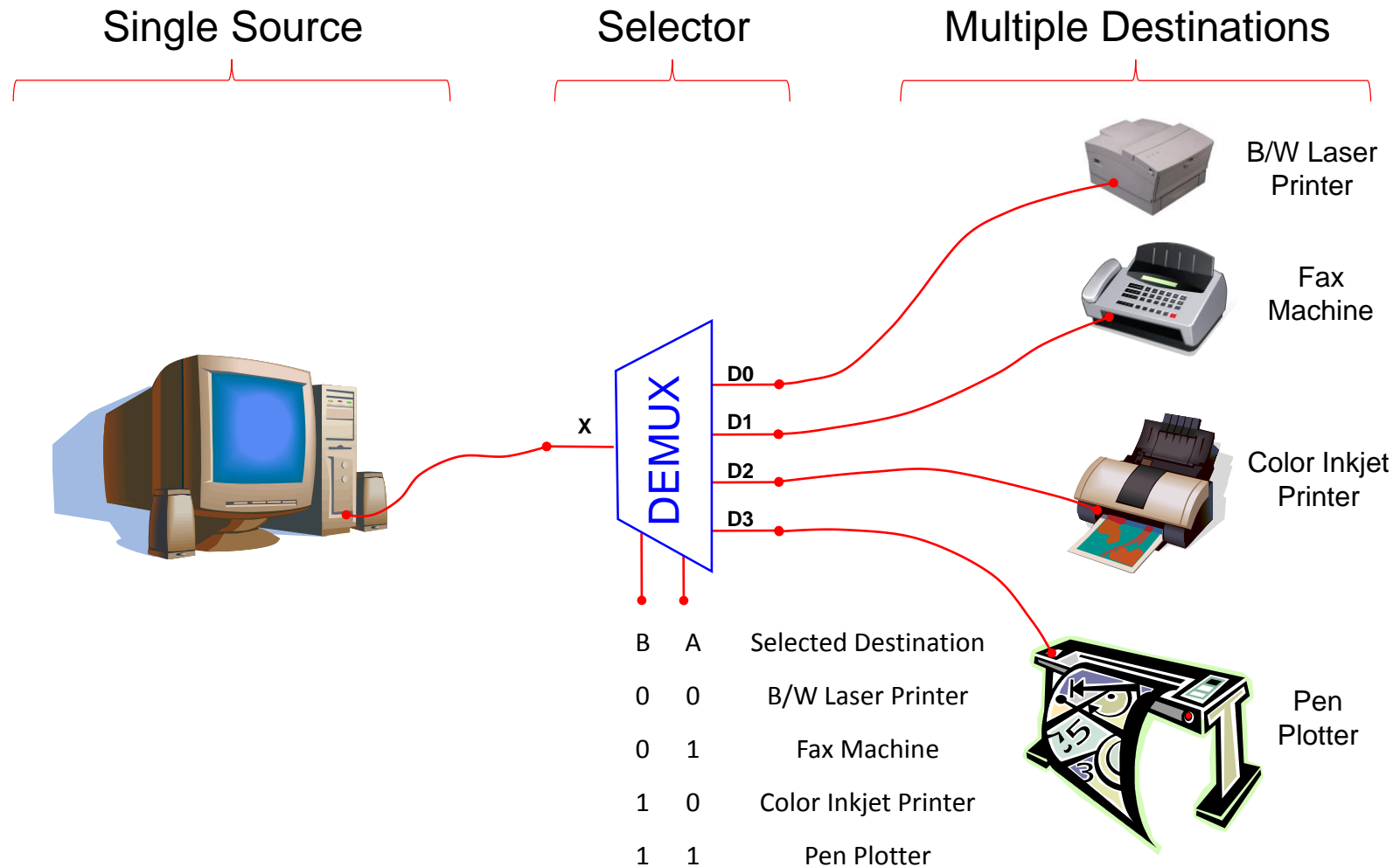

# 1-to-4 De-Multiplexer (DEMUX)

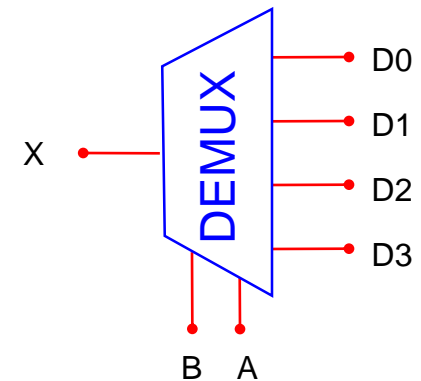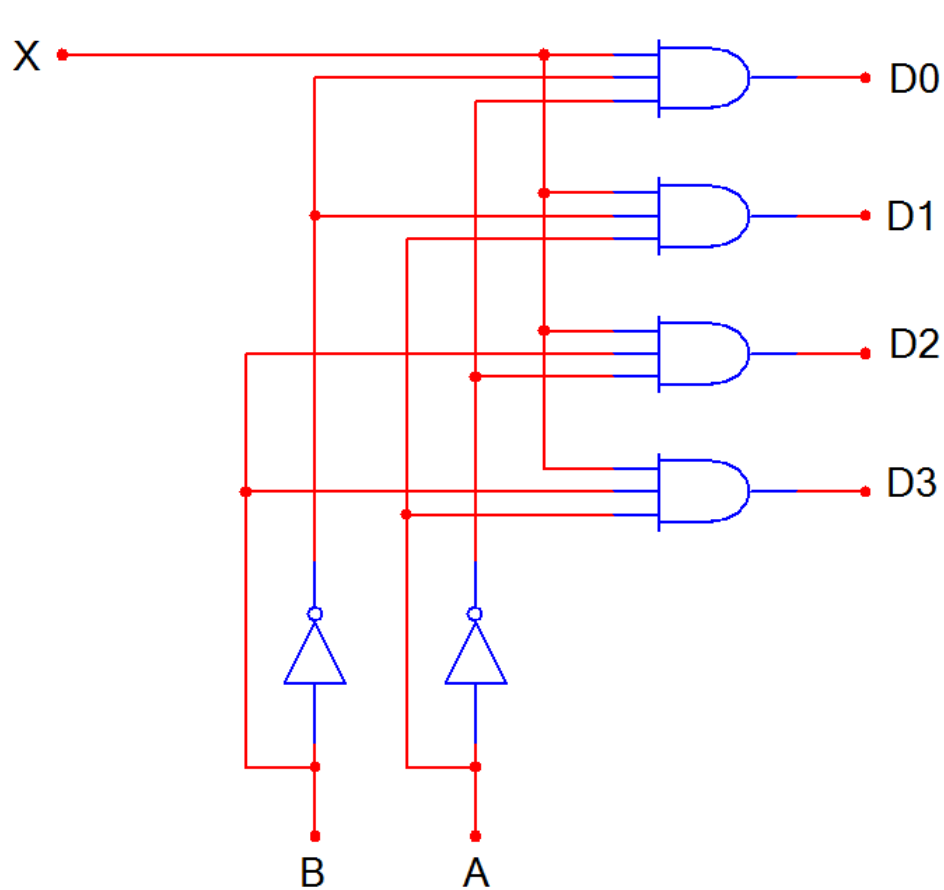

B	A	D0	D1	D2	D3
0	0	X	0	0	0
0	1	0	X	0	0
1	0	0	0	X	0
1	1	0	0	0	X

Thanks