



بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

In the name of Allah, the Most Merciful, the Most Kind

Date: 04-10-2021

BCS 103

Digital Logic & Computer Architecture

Lecture 17 and 18

Boolean Algebra


Boolean laws

Commutative law $AB = BA$ $A + B = B + A$	Absorption law $A + AB = A$ $A(A + B) = A$
Distributive law $A(B + C) = AB + BC$ $A + BC = (A + B)(A + C)$	De Morgan's law $\overline{A + B} = \overline{A} \bullet \overline{B}$ $\overline{A \bullet B} = \overline{A} + \overline{B}$
Associative law $A(BC) = (AB)C$ $A + (B + C) = (A + B) + C$	Note also $A + \overline{A}B = A + B$ $A(\overline{A} + B) = AB$

Laws of Boolean Algebra

- Commutative Law of Addition:


$$A + B = B + A$$

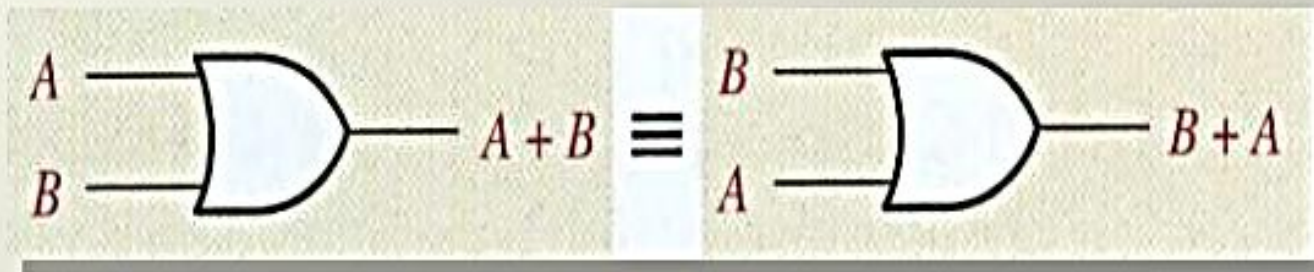

Laws of Boolean Algebra

- Commutative Law of Multiplication:


$$\mathbf{A * B = B * A}$$

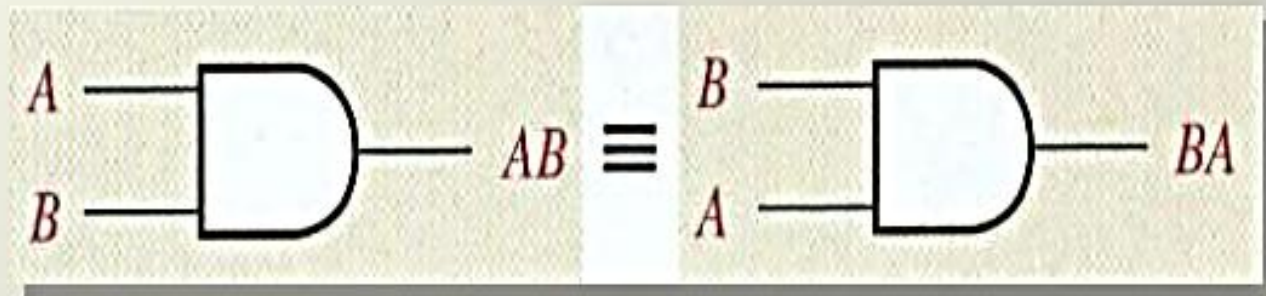

Laws of Boolean Algebra

- Associative Law of Addition:


$$\mathbf{A + (B + C) = (A + B) + C}$$

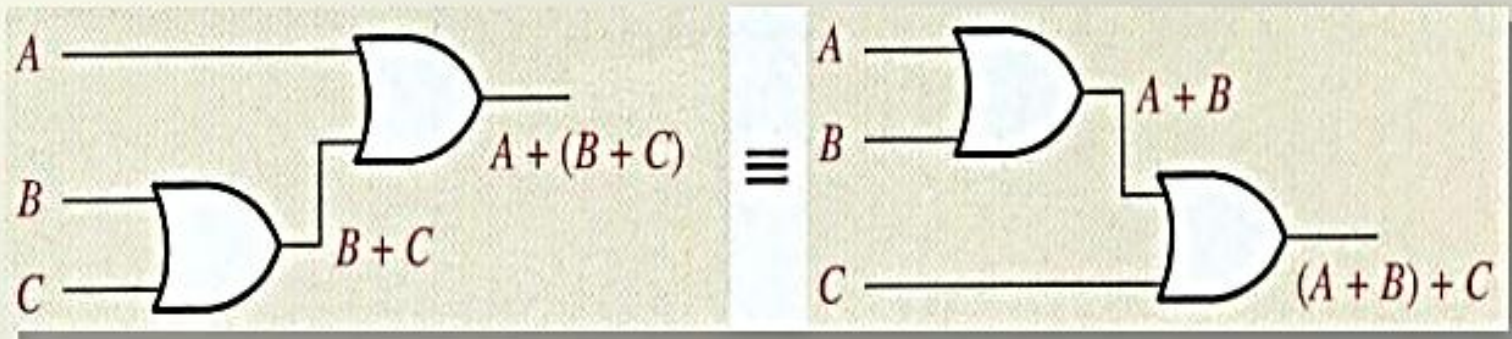

Laws of Boolean Algebra

- Associative Law of Multiplication:


$$A * (B * C) = (A * B) * C$$

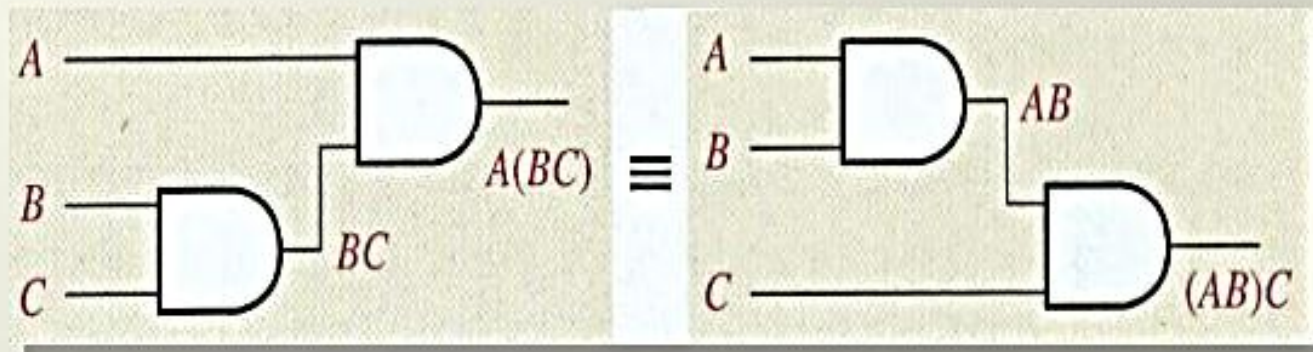

Laws of Boolean Algebra


- Distributive Law:

$$\mathbf{A(B + C) = AB + AC}$$

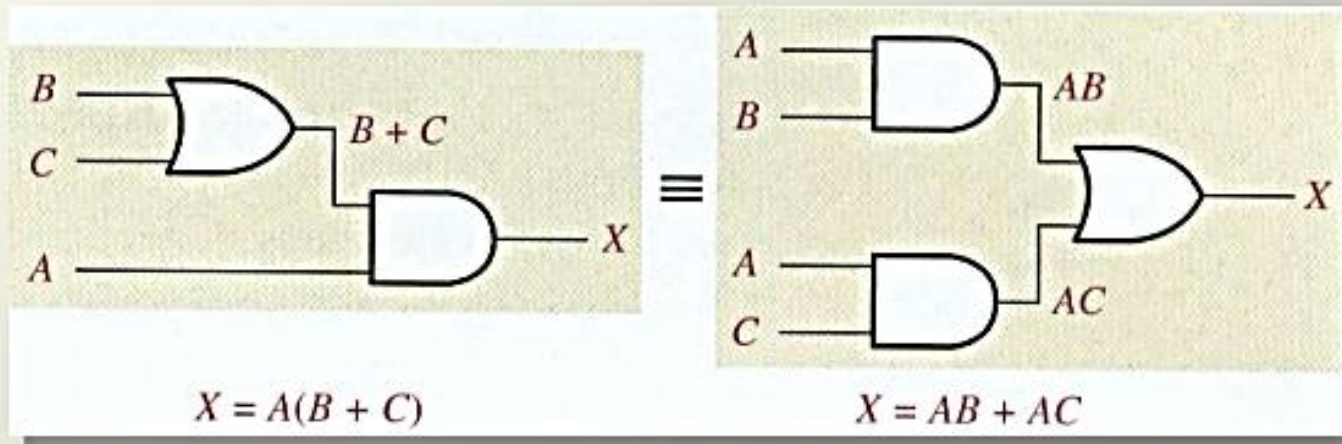

Rules of Boolean Algebra

- Rule 1 IDENTITY w.r.t ADDITION

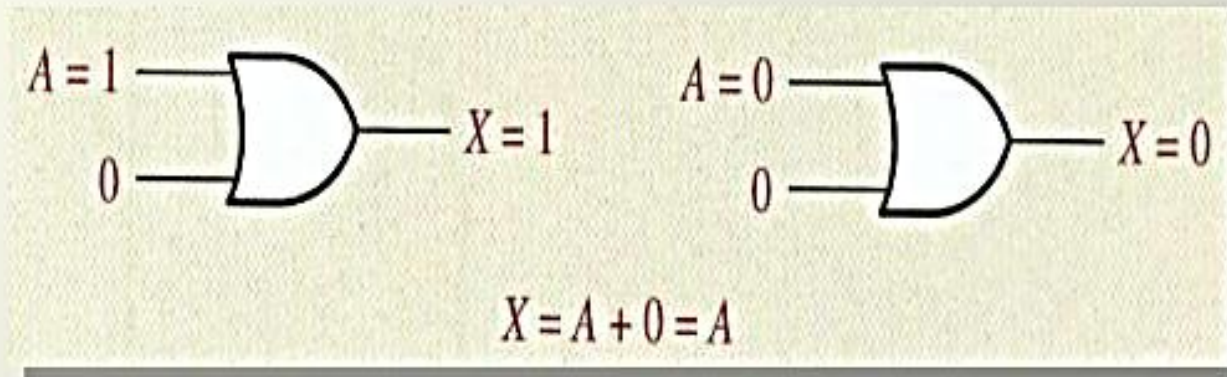


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

Rules of Boolean Algebra

- Rule 2 NULL w.r.t ADDITION

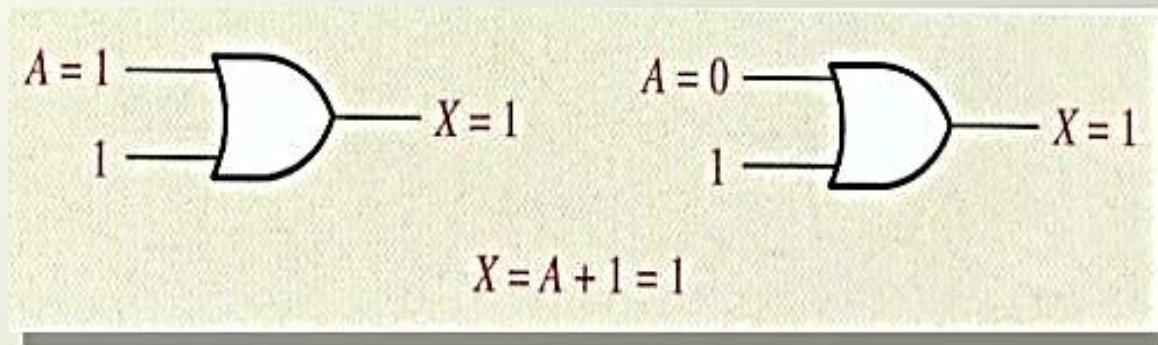


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

Rules of Boolean Algebra

- Rule 3 NULL w.r.t MULTIPLICATION

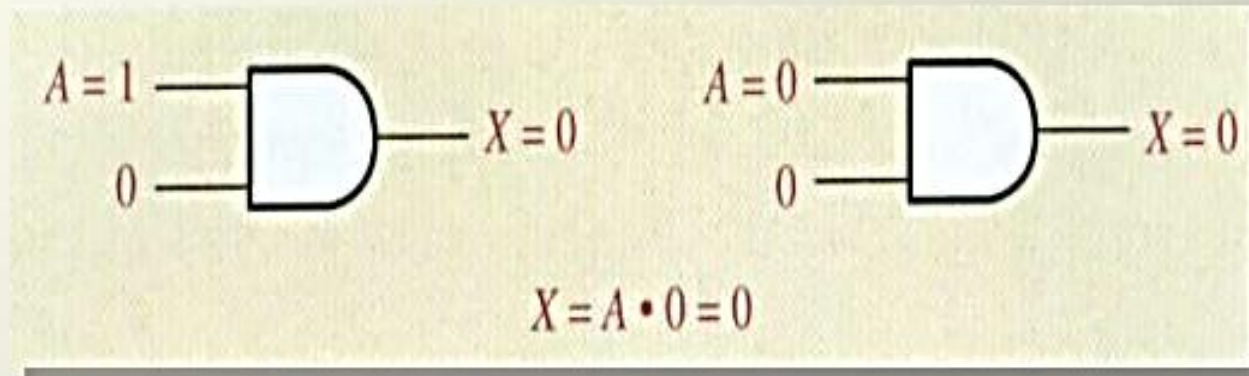


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

Rules of Boolean Algebra

- Rule 4 IDENTITY w.r.t MULTIPLICATION


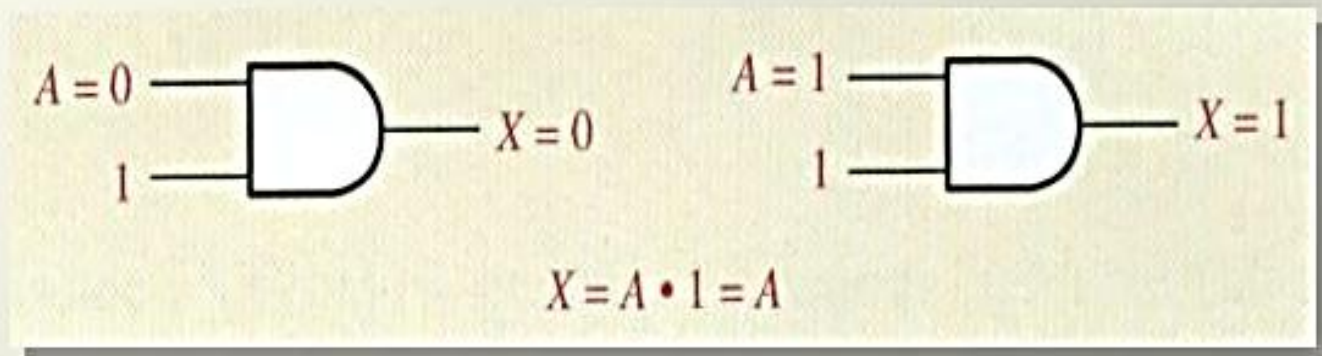


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

Rules of Boolean Algebra

- Rule 5 IDEMPOTENT w.r.t ADDITION

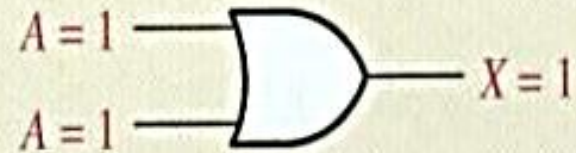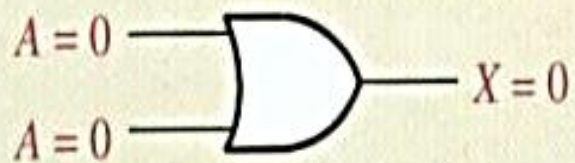


$$X = A + A = A$$

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

Rules of Boolean Algebra

- Rule 6 COMPLEMENTARITY w.r.t ADDITION

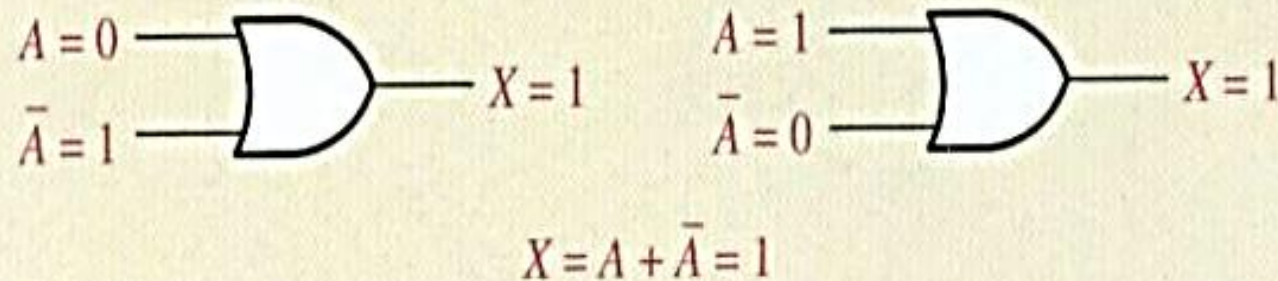


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

Rules of Boolean Algebra

- Rule 7 IDEMPOTENT w.r.t MULTIPLICATION

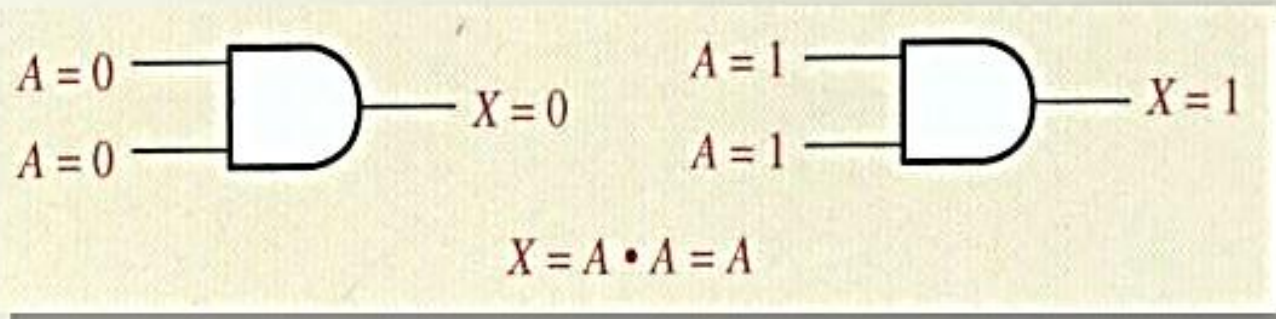


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

Rules of Boolean Algebra

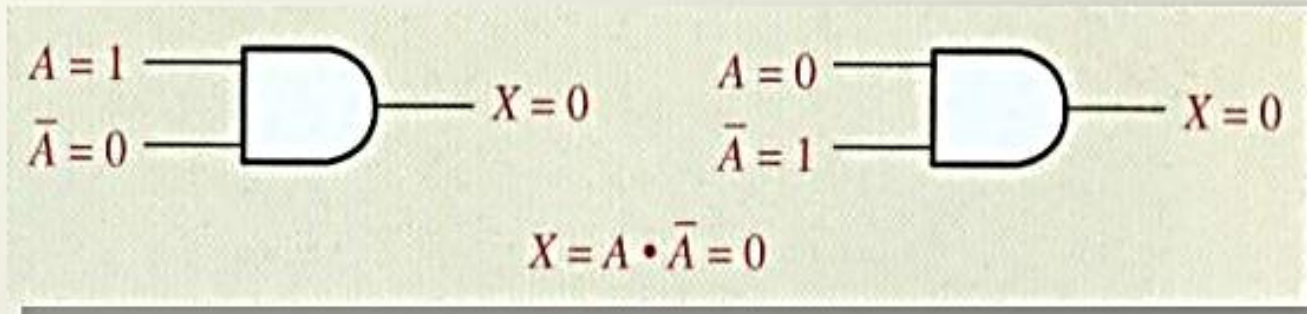- Rule 8 COMPLEMENTARITY w.r.t MULTIPLICATION




A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

Rules of Boolean Algebra

- Rule 9 INVOLUTION

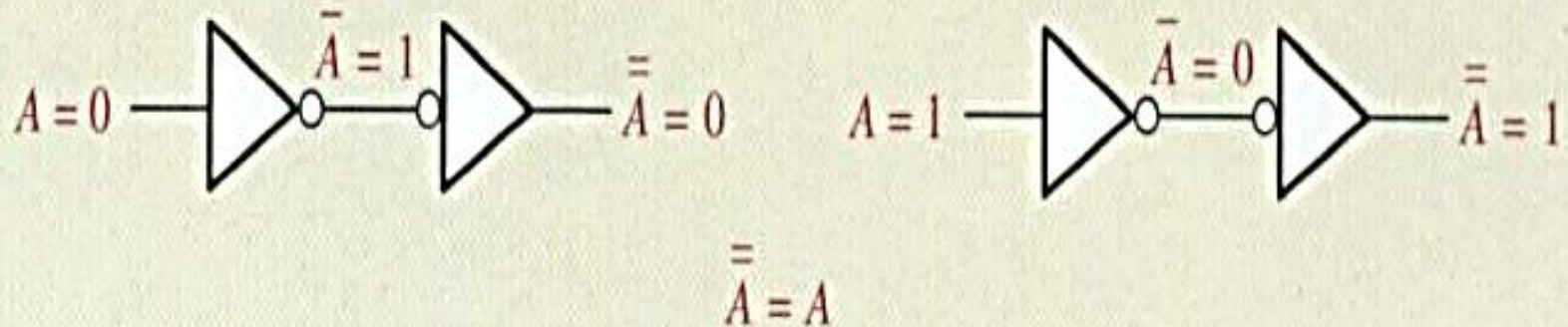


Rules of Boolean Algebra

- Rule 10: $A + AB = A$

A	B	AB	A + AB
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

↑ equal ↑

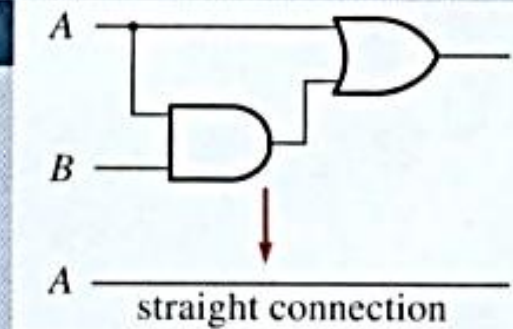

A	B	X	A	B	X
0	0	0	0	0	0
0	1	0	0	1	1
1	0	0	1	0	1
1	1	1	1	1	1


AND Truth Table OR Truth Table

Rules of Boolean Algebra

- Rule 11: $A + \overline{A}B = A + B$

A	B	$\overline{A}B$	$A + \overline{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

↑ equal ↑

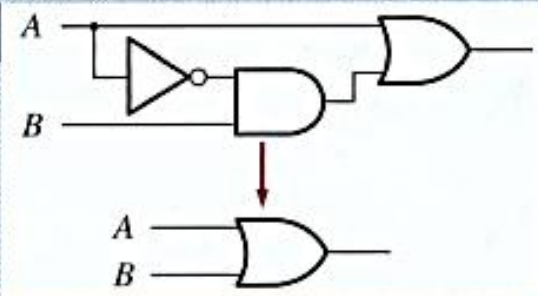

A	B	X	A	B	X
0	0	0	0	0	0
0	1	0	0	1	1
1	0	0	1	0	1
1	1	1	1	1	1


AND Truth Table OR Truth Table

Rules of Boolean Algebra

- Rule 12: $(A + B)(A + C) = A + BC$

A	B	C	A + B	A + C	(A + B)(A + C)	BC	A + BC
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

↑ equal ↑

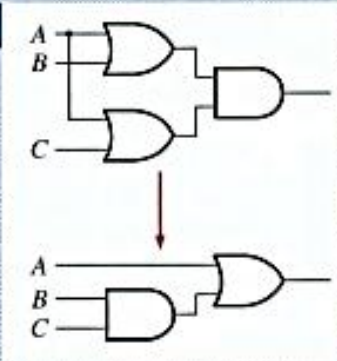

A	B	X	A	B	X
0	0	0	0	0	0
0	1	0	0	1	1
1	0	0	1	0	1
1	1	1	1	1	1

AND Truth Table OR Truth Table


DeMorgan's Theorem

DeMorgan's 1st Theorem

The complement of a product of variables is equal to the sum of the complemented variables.

$$\overline{AB} = \overline{A} + \overline{B}$$

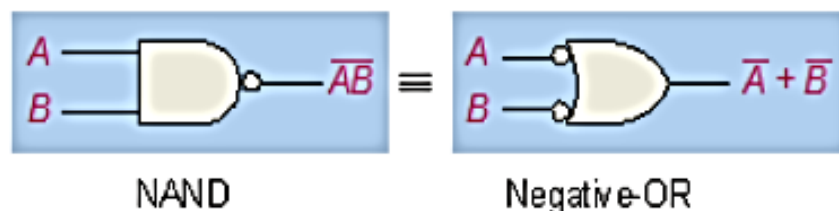Applying DeMorgan's first theorem to gates:



Inputs		Output	
A	B	\overline{AB}	$\overline{A} + \overline{B}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0


DeMorgan's Theorem

DeMorgan's 2nd Theorem

The complement of a sum of variables is equal to the product of the complemented variables.

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

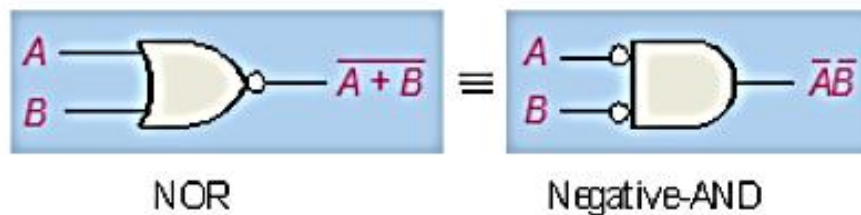Applying DeMorgan's second theorem to gates:



Inputs		Output	
A	B	$\overline{A + B}$	$\overline{A} \overline{B}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Simplification

Simplification

- Simplify the following expression

$$A + AB$$



Factoring A out of both terms

$$A(1 + B)$$



Applying identity $A + 1 = 1$

$$A(1)$$



Applying identity $1A = A$

$$A$$

Simplification


- Simplify the following expression

$$A + \bar{A}B$$



Applying the previous rule to expand A term
 $A + AB = A$

$$A + AB + \bar{A}B$$

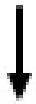

Factoring B out of 2nd and 3rd terms

$$A + B(A + \bar{A})$$



Applying identity $A + \bar{A} = 1$

$$A + B(1)$$



Applying identity $1A = A$

$$A + B$$

Simplification

- Simplify the following expression

$$(A + B)(A + C)$$



$$AA + AC + AB + BC$$



$$A + AC + AB + BC$$



$$A + AB + BC$$



$$A + BC$$

Distributing terms

Applying identity $AA = A$



Applying identity $A + AB = A$
to the $A + AC$ term

Applying identity $A + AB = A$
to the $A + AB$ term

Simplification

$$AB + A(B + C) + B(B + C)$$

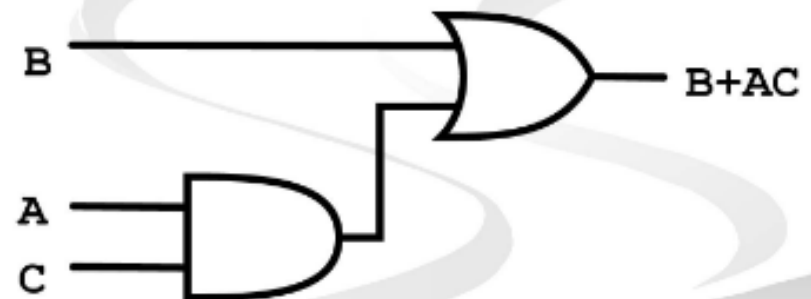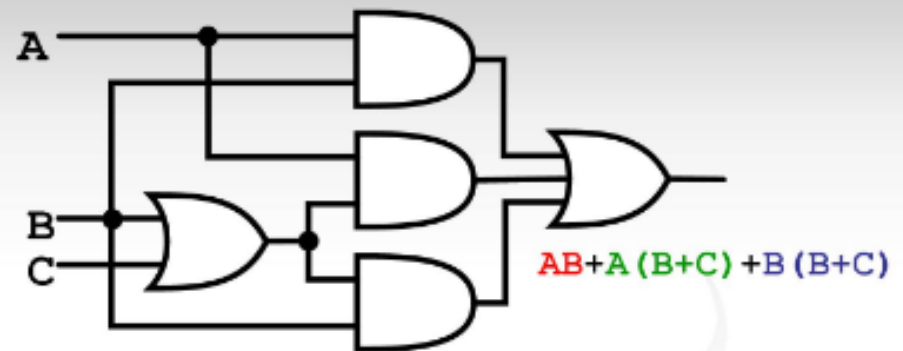- (distributive law)
 - $AB + AB + AC + BB + BC$
- (rule 7; $BB = B$)
 - $AB + AB + AC + \mathbf{B} + BC$
- (rule 5; $AB + AB = AB$)
 - $\mathbf{AB} + AC + B + BC$
- (rule 10; $B + BC = B$)
 - $AB + AC + \mathbf{B}$
- (rule 10; $AB + B = B$)
 - $\mathbf{B} + AC$



Simplification

- Simplify the following expression

Expression

$$\overline{AB}(\overline{A} + B)(\overline{B} + B)$$

$$\overline{AB}(\overline{A} + B)$$

$$(\overline{A} + \overline{B})(\overline{A} + B)$$

$$\overline{A} + \overline{B}B$$

$$\overline{A}$$

Rule(s) Used

Original Expression

Complement law, Identity law.

DeMorgan's Law

Distributive law. This step uses

Complement, Identity.

Simplification

- Simplify the following expression

Expression

$$(A + C)(AD + A\bar{D}) + AC + C$$

$$(A + C)A(D + \bar{D}) + AC + C$$

$$(A + C)A + AC + C$$

$$A((A + C) + C) + C$$

$$A(A + C) + C$$

$$AA + AC + C$$

$$A + (A + C)C$$

$$A + C$$

Rule(s) Used

Original Expression

Distributive.

Complement, Identity.

Commutative, Distributive.

Associative, Idempotent.

Distributive.

Idempotent, Identity, Distributive.

Identity, twice.

Simplification

- Simplify the following expression

Simplify: $\overline{A}(A + B) + (B + AA)(A + \overline{B})$:

Expression

$$\overline{A}(A + B) + (B + AA)(A + \overline{B})$$

$$\overline{A}A + \overline{A}B + (B + A)A + (B + A)\overline{B}$$

$$\overline{A}B + (B + A)A + (B + A)\overline{B}$$

$$\overline{A}B + BA + AA + B\overline{B} + A\overline{B}$$

$$\overline{A}B + BA + A + A\overline{B}$$

$$\overline{A}B + AB + AT + A\overline{B}$$

$$\overline{A}B + A(B + T + \overline{B})$$

$$\overline{A}B + A$$

$$A + \overline{A}B$$

$$(A + \overline{A})(A + B)$$

$$A + B$$

Rule(s) Used

Original Expression

Idempotent (AA to A), then Distributive, used twice.

Complement, then Identity. (Strictly speaking, we also used the Commu

Distributive, two places.

Idempotent (for the A 's), then Complement and Identity to remove $B\overline{B}$.

Commutative, Identity; setting up for the next step.

Distributive.

Identity, twice (depending how you count it).


Commutative.

Distributive.

Complement, Identity.


Generate Equation

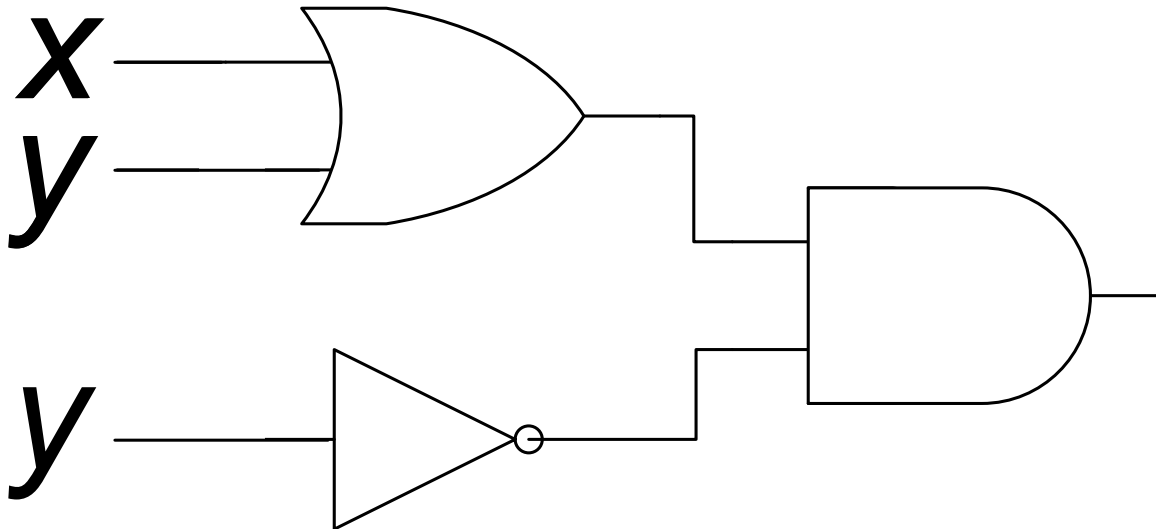- Find the output of the following circuit




Generate Equation

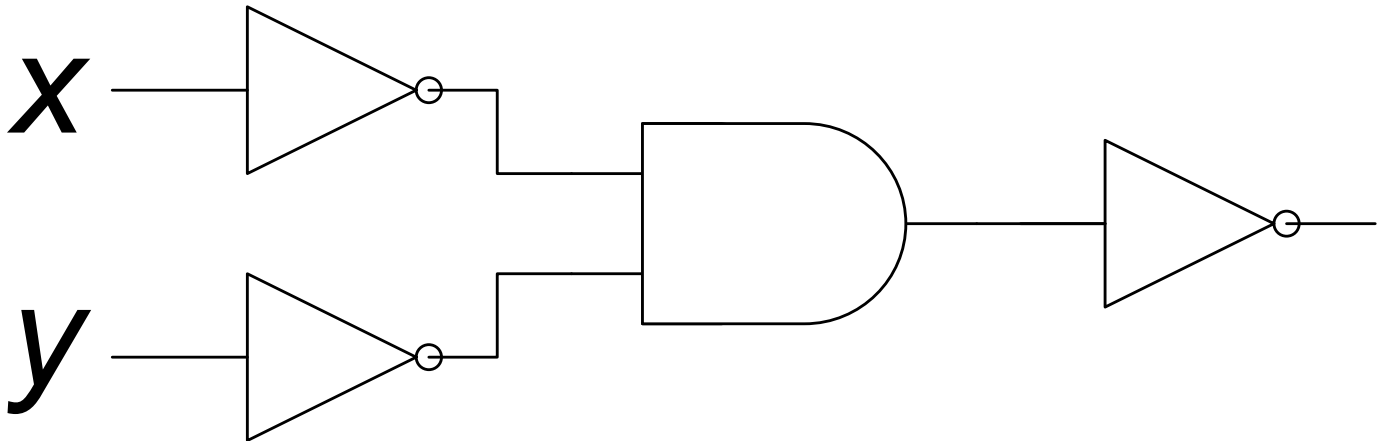- Find the output of the following circuit




Generate Equation

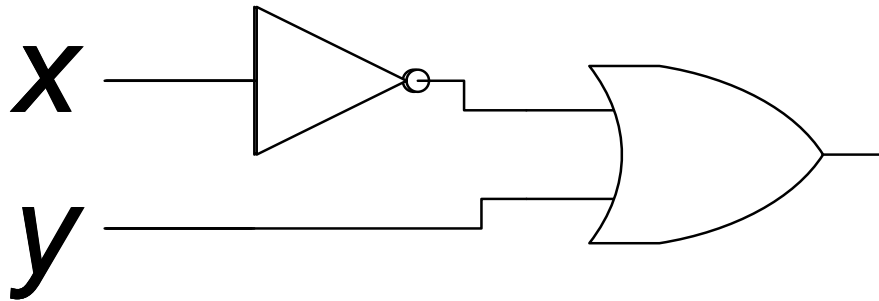- Find the output of the following circuit




Generate Equation

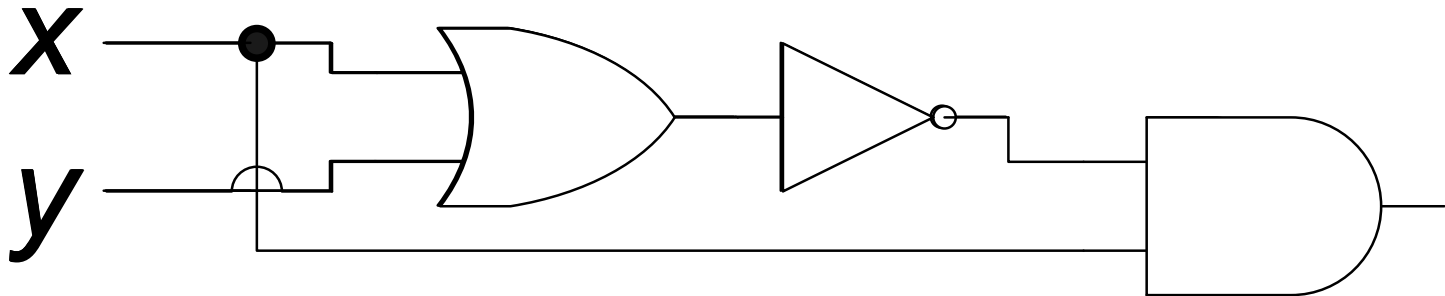- Find the output of the following circuit




Generate Equation

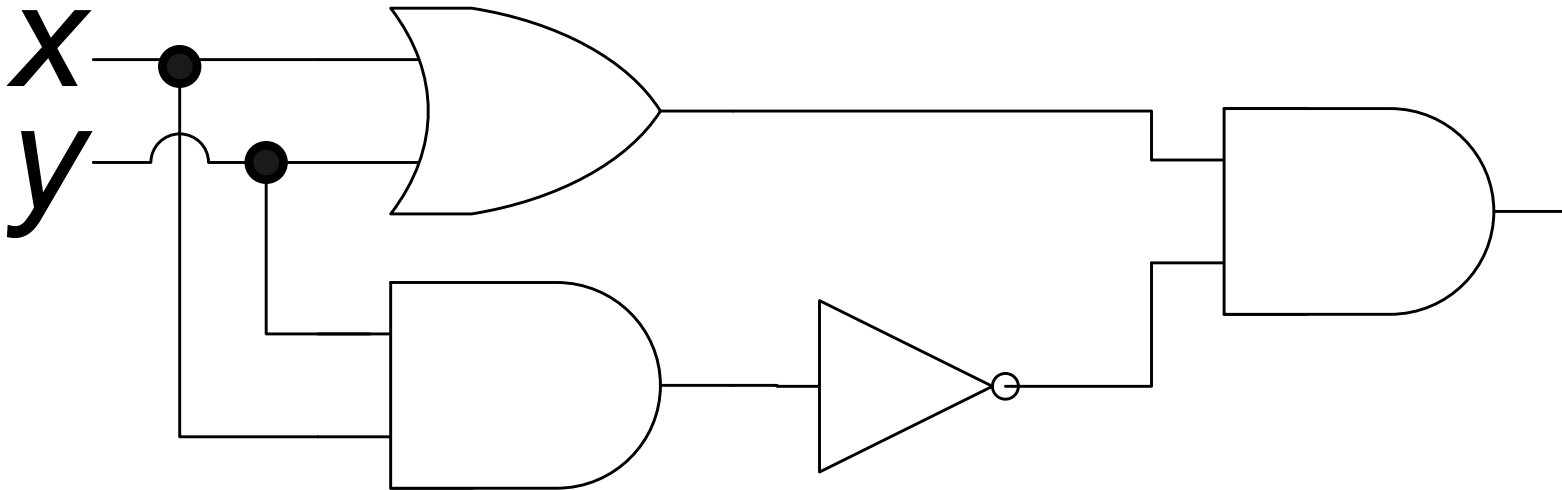- Find the output of the following circuit




Generate Equation

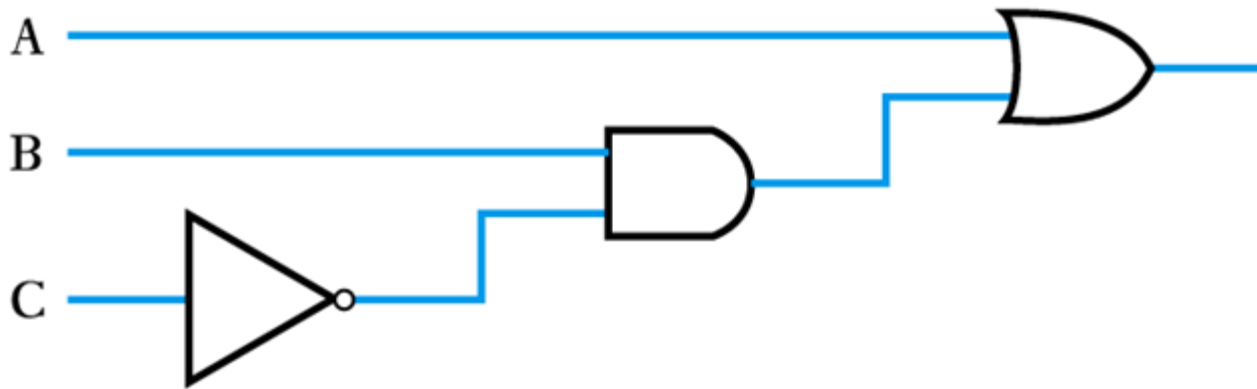- Find the output of the following circuit




Generate Equation

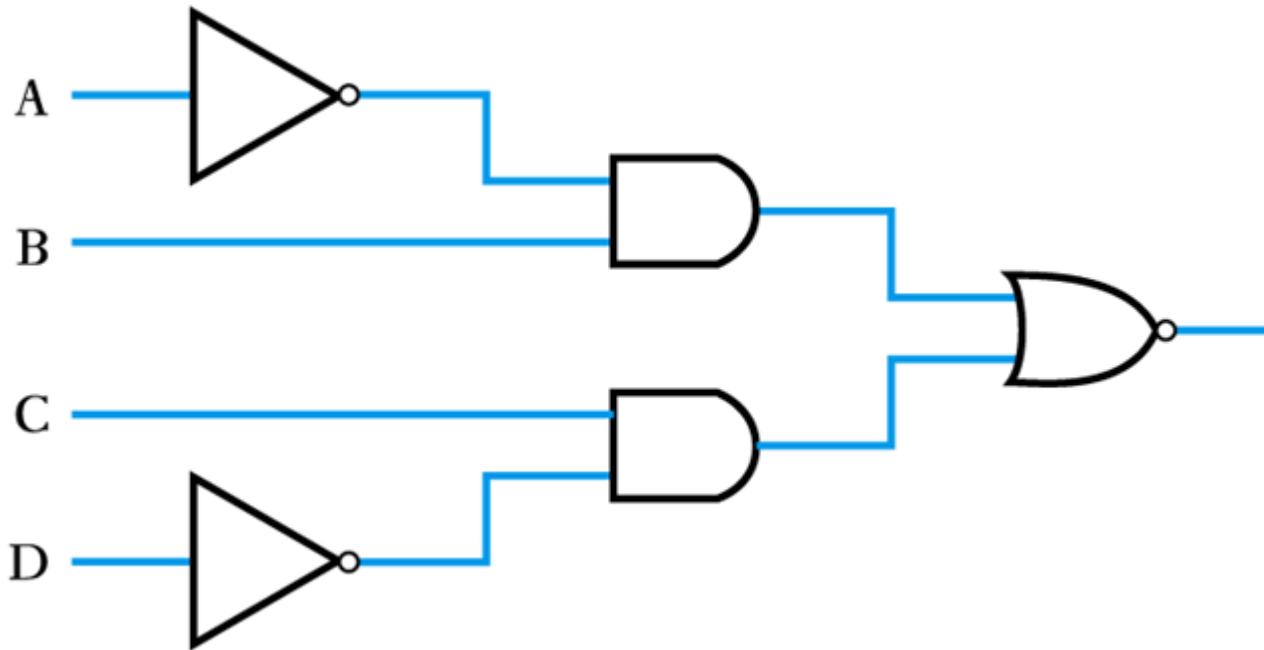- Find the output of the following circuit




Generate Equation

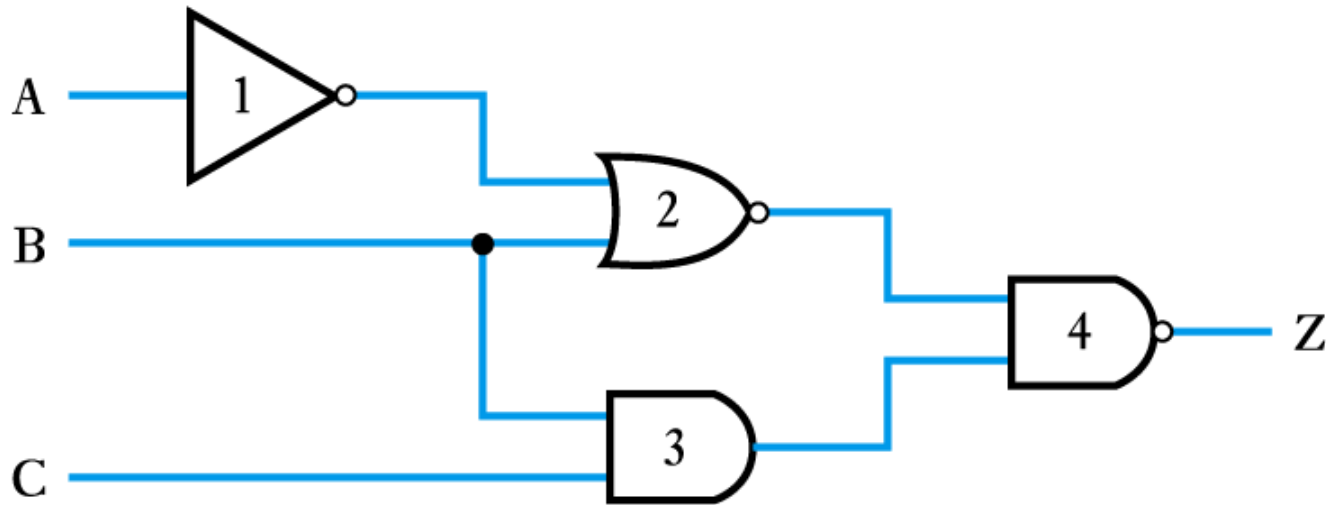- Find the output of the following circuit




Generate Equation

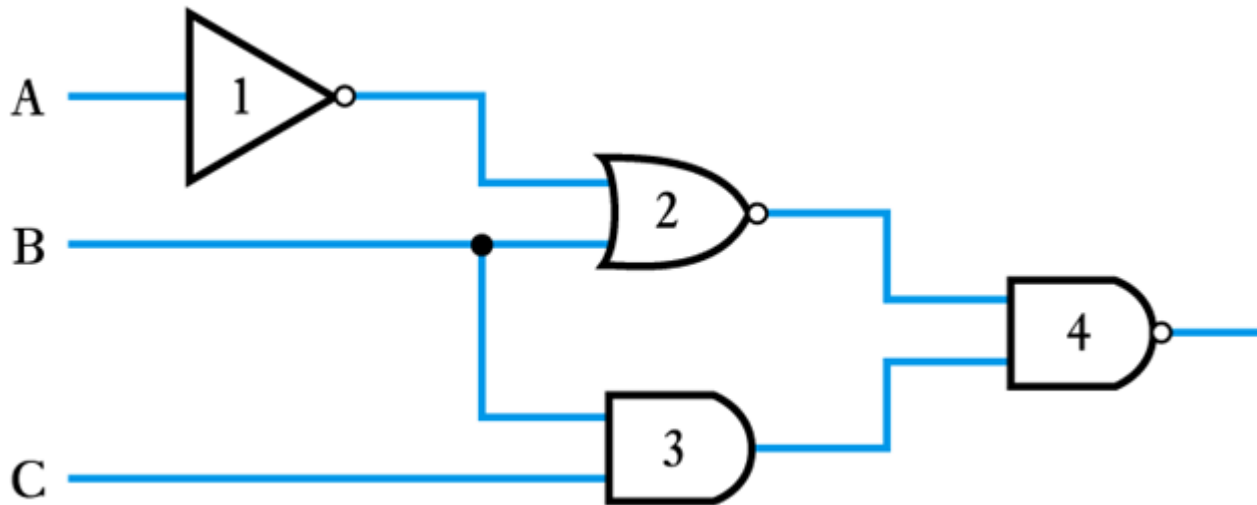- Find the output of the following circuit



Generate Equation

- Find the output of the following circuit

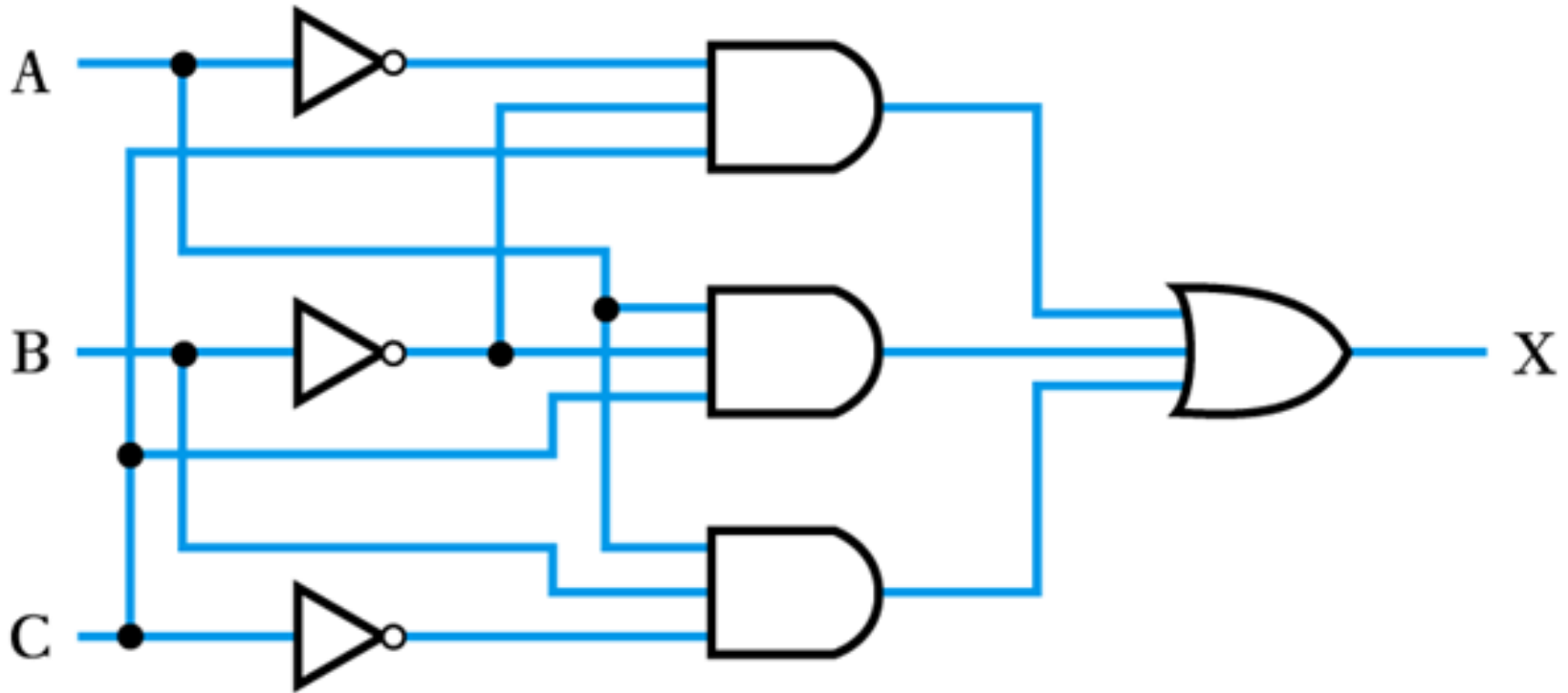

Example 1

Determine if the following equation is valid

$$\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2 = \bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3$$

Left-Hand Side (LHS)

Row number	x_1	x_2	x_3	$\overline{x_1} \overline{x_3}$	$x_2 x_3$	$\overline{x_1} x_2$	f
0	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
2	0	1	0	1	0	0	1
3	0	1	1	0	1	0	1
4	1	0	0	0	0	1	1
5	1	0	1	0	0	1	1
6	1	1	0	0	0	0	0
7	1	1	1	0	1	0	1

Right-Hand Side (RHS)

Row number	x_1	x_2	x_3	$\overline{x_1 x_2}$	$x_1 x_3$	$\overline{x_2} \overline{x_3}$	f
0	0	0	0	0	0	1	1
1	0	0	1	0	0	0	0
2	0	1	0	1	0	0	1
3	0	1	1	1	0	0	1
4	1	0	0	0	0	1	1
5	1	0	1	0	1	0	1
6	1	1	0	0	0	0	0
7	1	1	1	0	1	0	1

$$\underbrace{\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2}_{\text{LHS}} \stackrel{?}{=} \underbrace{\bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3}_{\text{RHS}}$$

f
1
0
1
1
1
1
0
1

f
1
0
1
1
1
1
0
1

Thanks